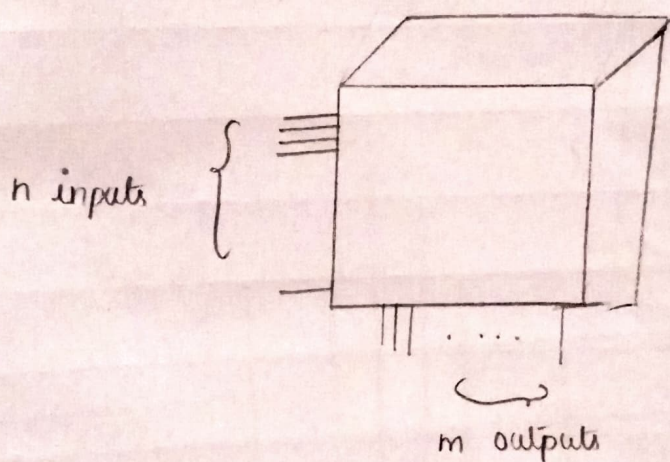


Encoder:

\* An encoder converts an active input signals into a coded output signal.

\* There are  $n$  input lines, only one of which is active.

\* Internal logic within the encoder converts this active input to a coded binary output with  $m$  bits.



Decimal to BCD Encoder

\* It is a common type of encoder. The decimal-to-BCD encoder. The switches are push-button switches like those of a pocket calculator.

\* When button 3 is pressed, the C and D OR gate have high inputs, therefore, the output is

$$ABCD = 0011$$




If button 5 is Pressed, the outcome is

$$ABCD = 0101$$

when switch 9 is Pressed,

$$ABCD = 1001$$

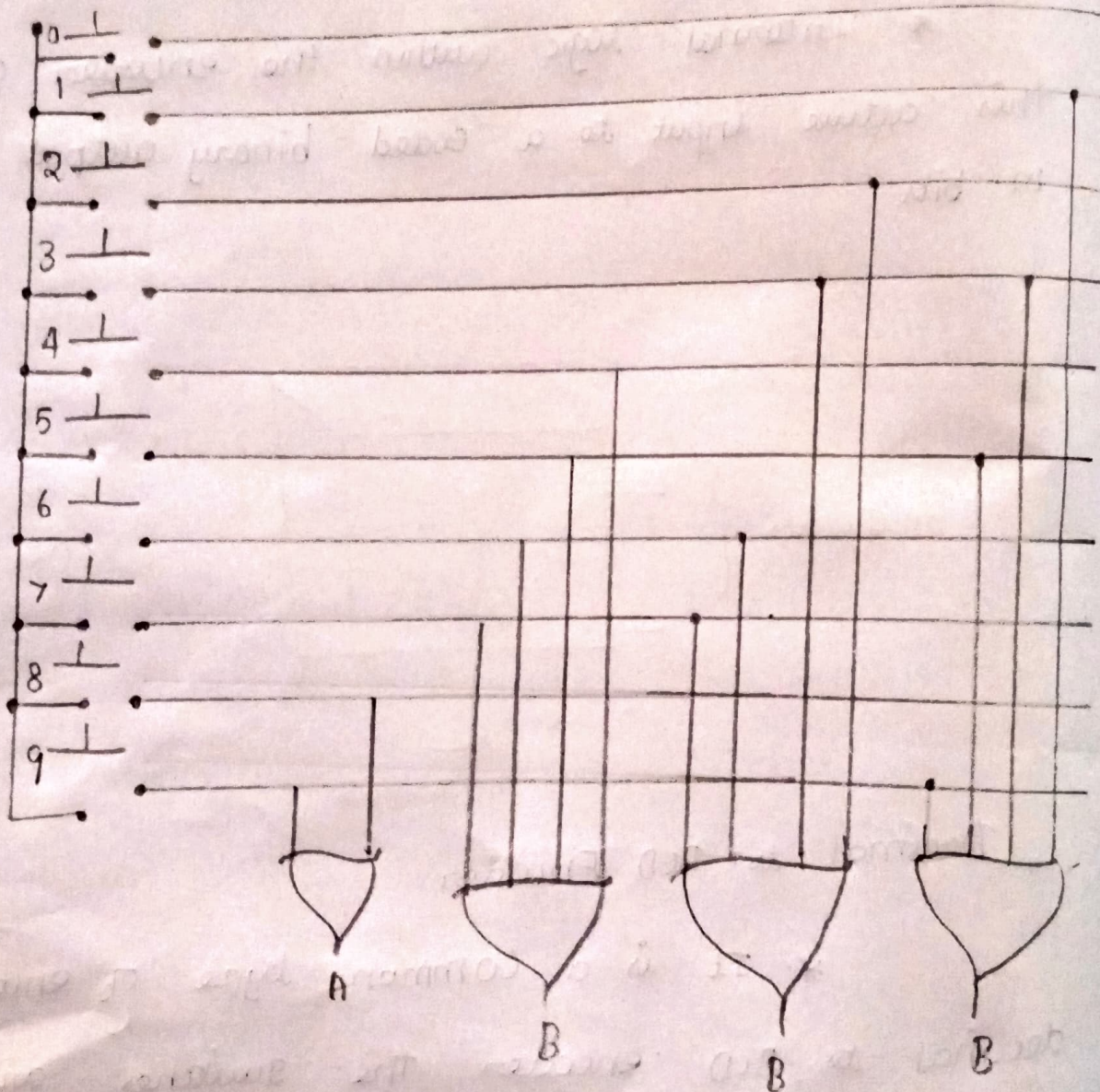

Decimal to BCD Encoder